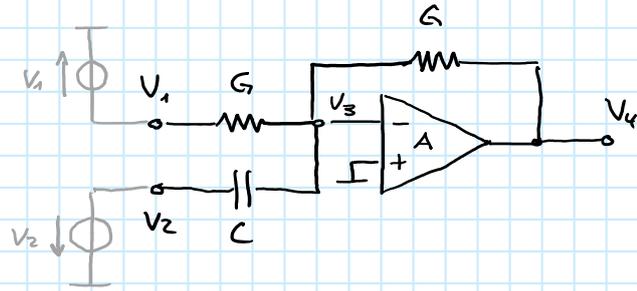


# Signal-Flow Graphs in 12 Short Lessons

## Exercise for Episode 4

Hanspeter Schmid, FHNW/IME

The circuit shown on the right has two input voltage sources. Draw all circuits that occur under source superposition, then draw the signal-flow graph, and calculate  $V_4$  for  $A \rightarrow \infty$ .




# Signal-Flow Graphs in 12 Short Lessons
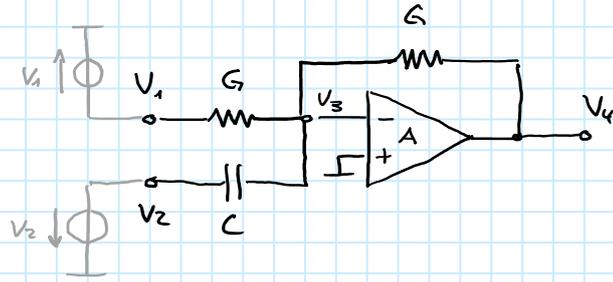
## Solution for Episode 4

Hanspeter Schmid, FHNW/IME


The circuit shown on the right has two input voltage sources. Draw all circuits that occur under source superposition, then draw the signal-flow graph, and calculate  $V_4$  for  $A \rightarrow \infty$ .



Solution Remember that the output of the OpAmp also is a voltage source.


Then:

$$V_1 \neq 0 \\ V_2 = V_4 = 0$$

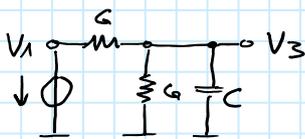


$$\frac{V_3}{V_1} = \frac{G}{2G + sC} = t_{13}$$

$$V_2 \neq 0 \\ V_1 = V_4 = 0$$

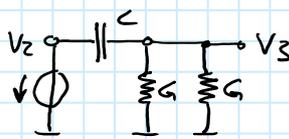


$$\frac{V_3}{V_2} = \frac{sC}{2G + sC} = t_{23}$$

$$V_4 \neq 0 \\ V_1 = V_2 = 0$$

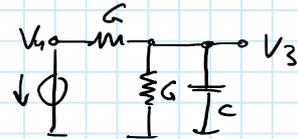

$$\frac{V_3}{V_4} = \frac{G}{2G + sC} = t_{43}$$

Graph:

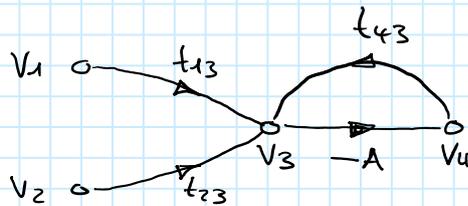

Mason:

$$\frac{V_4}{V_1} = - \frac{A t_{13}}{1 + A t_{43}} \stackrel{A \rightarrow \infty}{\approx} - \frac{t_{13}}{t_{43}} = -1 = T_{14}$$

$$\frac{V_4}{V_2} = - \frac{A t_{23}}{1 + A t_{43}} \stackrel{A \rightarrow \infty}{\approx} - \frac{t_{23}}{t_{43}} = - \frac{sC}{G} = T_{24}$$

Superposition again:

$$V_4 = V_1 T_{14} + V_2 T_{24} = - \left( V_1 + \frac{sC}{G} V_2 \right)$$

This circuit adds the differentiated  $V_2$  to  $V_1$ .